
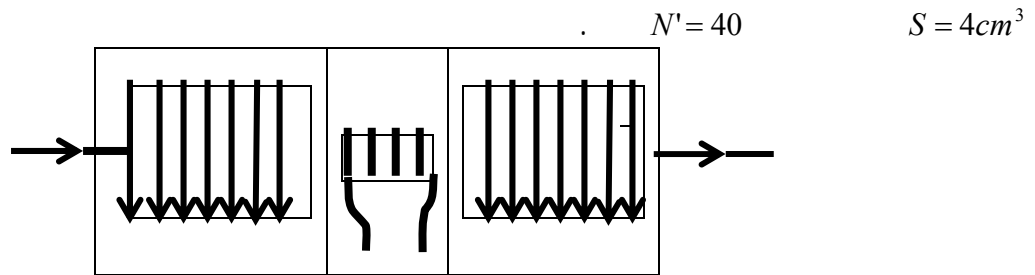


500 (I)

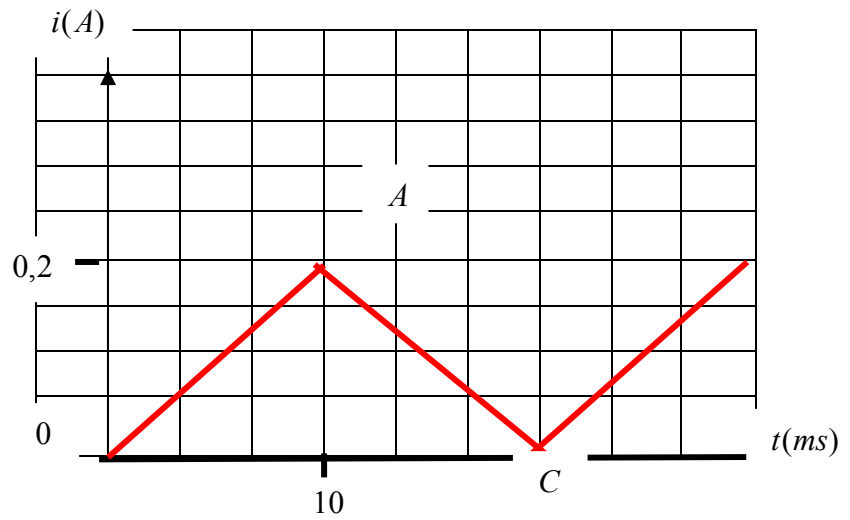

$t = 20ms$       $t = 0$

-1

-2

-3

$t = 20ms$       $t = 0$  :

-4


$e$       $i$  :

1div  $\longrightarrow$  0,1mV :  $e$  :

4div  $\longrightarrow$  0,2A :  $i$  :

3div  $\longrightarrow$  10mA :  $t$  :

(1)

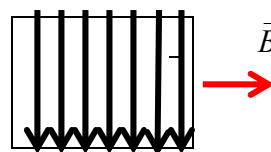

$$B = \mu_0 \cdot n \cdot i$$

: [0,10ms] (2)

$$i = a.t$$

:

$i$

: [O, A]

$a$

$$a = \frac{\Delta i}{\Delta t} = \frac{i(A) - i(O)}{t(A) - t(O)} = \frac{0,2A}{10 \times 10^{-3}s} = 20A/s$$

$$i = 20.t$$

:

$$: [10, 20ms] \quad \text{_____} \quad (3)$$

$$i = \alpha.t + \beta$$

:

$i$

: [A, C]

$\alpha$

$$\alpha = \frac{\Delta i}{\Delta t} = \frac{i(C) - i(A)}{t(C) - t(A)} = \frac{(0 - 0,2)A}{(20 - 10) \times 10^{-3}s} = -20A/s$$

$$i = -20t + \beta$$

:

:

$$t = 20ms$$

$$. [10, 20ms]$$

$\beta$

$$i = 0$$

$$0 = -20 \times (20 \times 10^{-3}s) + \beta$$

$$\beta = 0,4$$

:

$$i = -20t + 0,4$$

:

:

(3)

$$\Phi = N'.B.S' = N'.S'.\mu_0.n.i = 40 \times 4 \times 10^{-4} \times 4 \times \pi \times 10^{-7} \times 500 \times i = 10^{-5} \times i$$

$$\Phi = 10^{-5} i$$

:

$$e = -\frac{d\Phi}{dt}$$

:

$$e = -\frac{d\Phi}{dt} = -\frac{d(10^{-5}.i)}{dt} = -10^{-5} \times \frac{di}{dt}$$

:

$$\frac{di}{dt} = 20$$

:

$$i = 20.t$$

$$: [0, 10ms] :$$

\_\_\_\_\_

$$e = -10^{-5} \times 20 = 2 \times 10^{-4}V = -0,2 \times 10^{-3}V = -0,2mV$$

:

$$: [10, 20ms] :$$

\_\_\_\_\_

$$\frac{di}{dt} = -20$$

:

$$i = -20.t + 0,4$$

$$e = -10^{-5}(-20) = 2 \times 10^{-4} = 0,2 \times 10^{-3}V = 0,2mV$$

:

:

$e$

(4)

$$1div \longrightarrow 0,1mV$$


:  $e$  :

$$4div \longrightarrow 0,2A$$


:  $i$  :

$$3div \longrightarrow 10mA$$

:  $t$  :

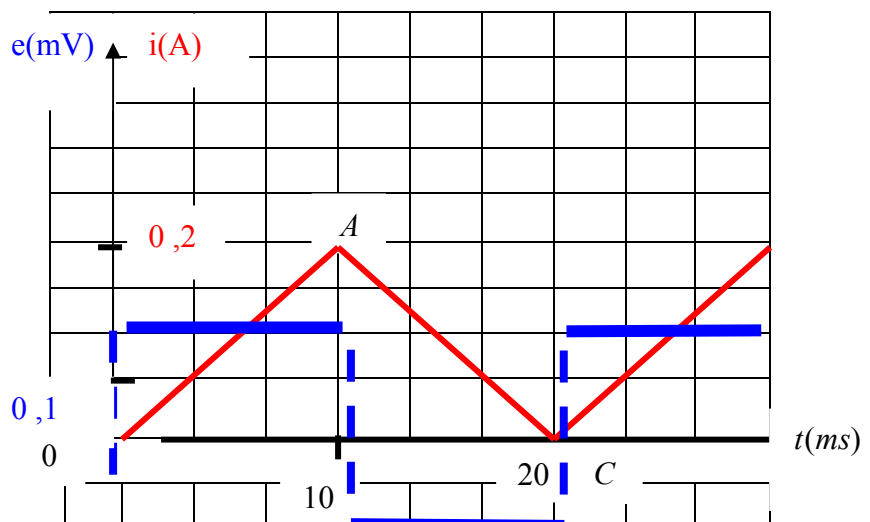

$$L = 0,1H$$

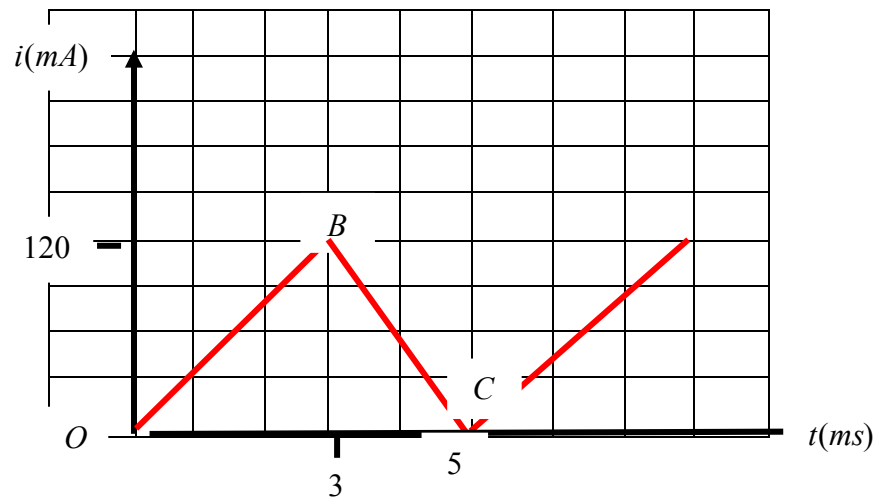

$$e \quad (1)$$

$$e \quad (1)$$

$$e \quad (2)$$

$$e = -L \frac{di}{dt} \quad (1)$$

$$[0,3ms] \quad \frac{e}{i} \quad (2)$$

:

$$a = \frac{\Delta i}{\Delta t} = \frac{i_B - i_O}{t_B - t_O} = \frac{(120 - 0) \times 10^{-3} A}{(3 - 0) \times 10^{-3} s} = 40 A/s$$

$$i = 40t :$$

$$e = -L \frac{di}{dt} = -0,1 \times 40 = -4V :$$

$$\frac{di}{dt} = 40 :$$

$$e = -4V$$

:

$$[3ms,5ms] \quad \frac{e}{i}$$

:

$$i = \alpha t + \beta :$$

$$\alpha = \frac{\Delta i}{\Delta t} = \frac{i_C - i_B}{t_C - t_B} = \frac{(0 - 120) \times 10^{-3} A}{(5 - 3) \times 10^{-3} s} = -60 A/s$$

$$i = -60t + \beta :$$

$$[3ms,5ms]$$

β

$$i = 0 : \quad t = 5ms = 5 \times 10^{-3} s :$$

$$0 = -60 \times (5 \times 10^{-3}) + \beta :$$

$$\beta = 0,3$$

:



$$0 = -0,3 + \beta :$$

$$i = -60t + 0,3$$

:

$$\frac{di}{dt} = -60$$
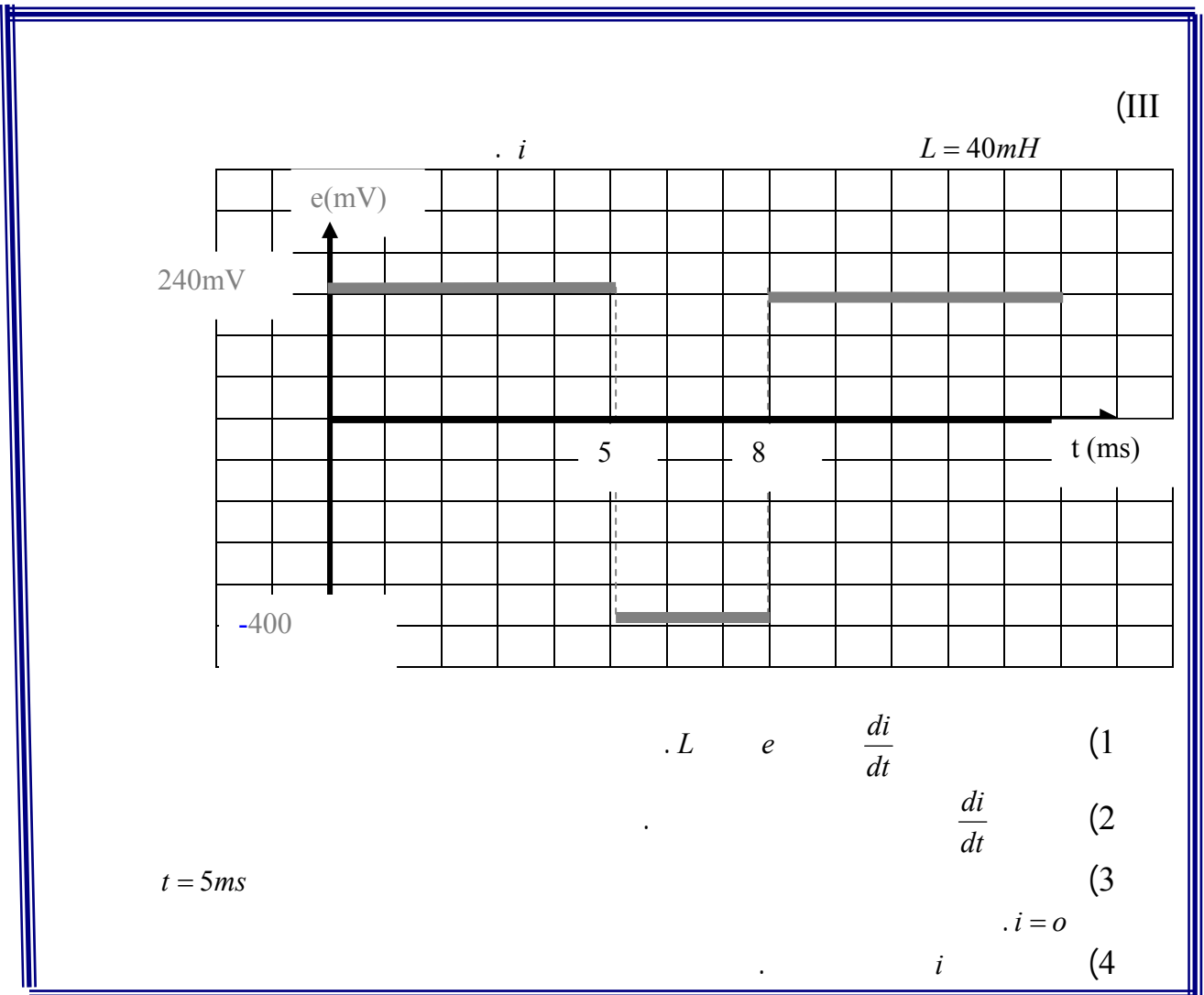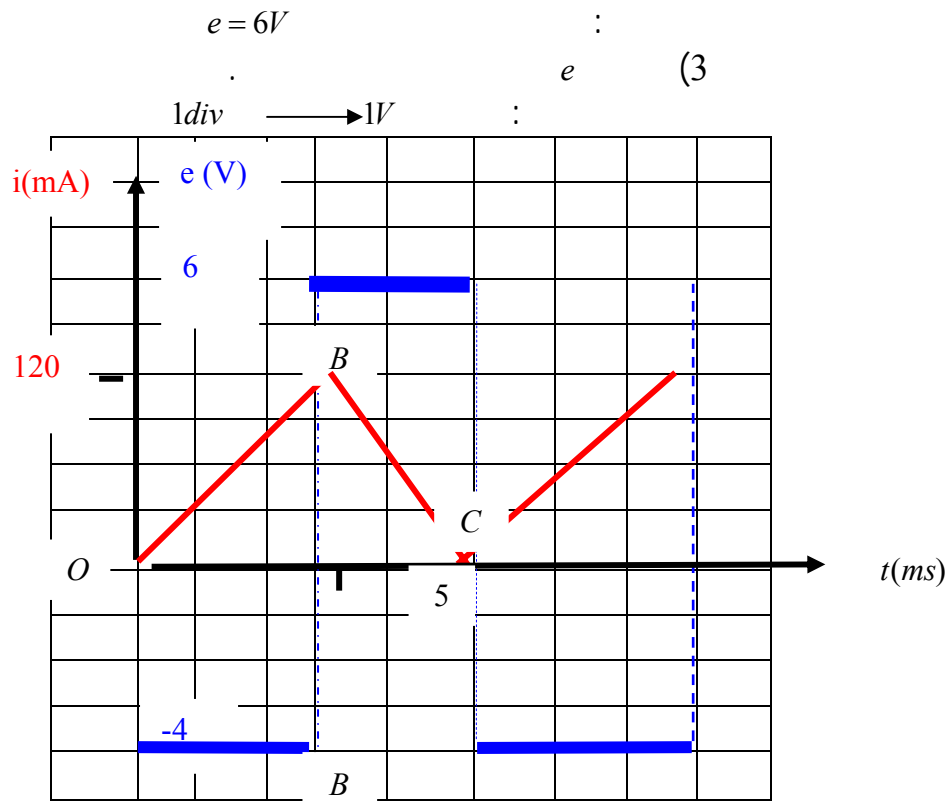
$$e = -L \frac{di}{dt} = -0,1 \times (-60) = 6V :$$



$$\frac{di}{dt} = -\frac{e}{L} \quad ; \quad e = -L \frac{di}{dt} \quad (1)$$

$$e = 240mV = 0,24V \quad : \quad [0,5ms] : \underline{\hspace{2cm}} \quad (2)$$

$$\frac{di}{dt} = -\frac{e}{L} = -\frac{0,24}{0,04} = -6 \quad :$$

$$e = -400mV = -0,4V \quad :$$

$$[5ms,8ms] : \underline{\hspace{2cm}}$$

$$\frac{di}{dt} = -\frac{e}{L} = -\frac{-0,4}{0,04} = 10 \quad :$$

$$\frac{di}{dt} = -6 \quad : \quad : \quad [0,5ms] : \underline{\hspace{2cm}} \quad (3)$$

$$i = -6t + k \quad :$$

$$. i = 0 \quad t = 5ms \quad :$$

$$k = 0,03 \quad : \quad 0 = -6 \times (5 \times 10^{-3}) + k \quad :$$

$$i = -6t + 0,03 \quad : \quad [0,5ms] \quad \underline{\hspace{2cm}} \quad i \quad \underline{\hspace{2cm}}$$

$$\frac{di}{dt} = 10 \quad : \quad [5,8ms] \quad \underline{\hspace{2cm}}$$

$$i = 10t + k' \quad :$$

$$. i = 0 \quad t = 5ms \quad :$$

$$k' = -0,05 \quad : \quad 0 = 10(5 \times 10^{-3}) + k'$$

$$i = 10t - 0,05 \quad : \quad [5,8ms] \quad \underline{\hspace{2cm}} \quad i \quad \underline{\hspace{2cm}}$$

$$: \quad (5)$$

$$[0,5ms]$$


$$i = -6t + 0,03 \quad :$$

$i$

$t(ms)$	0	5
$i(mA)$	30	0

$$1div \quad \longrightarrow \quad 1ms \quad :$$
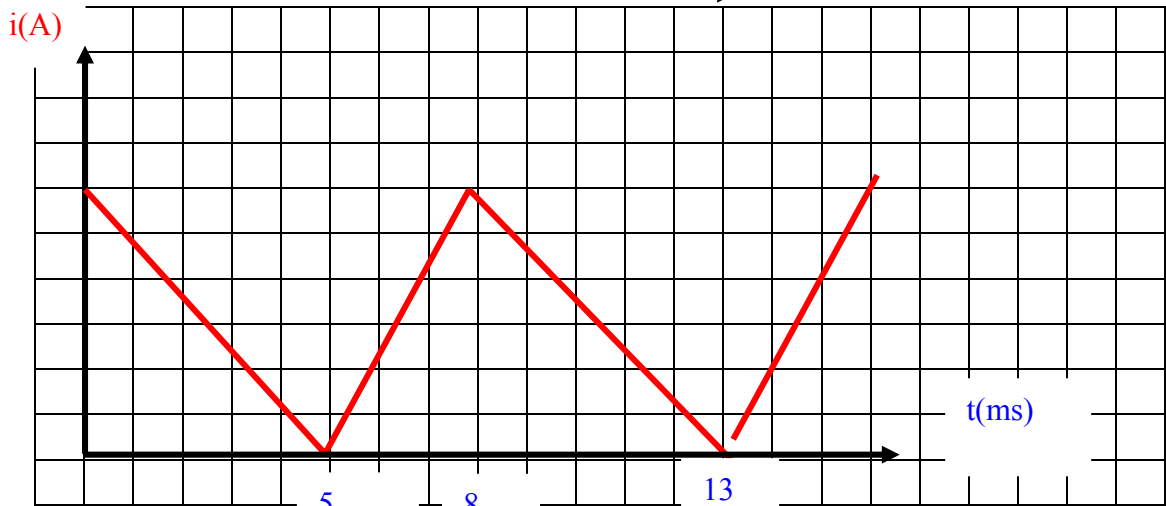
$$2div \quad \longrightarrow \quad 10mA$$



$$[5ms,8ms]$$

$$i = 10t - 0,05 \quad :$$

$i$

$t(ms)$	5	8
$i(mA)$	0	30

(III)

$N = 1000$

$\ell = 1m$

(A,C)

$r = 5cm$

.C A

$I = 5A$  :

(1)

. $\vec{B}$


(1-1

(2-1

L

(3-1

(4-1

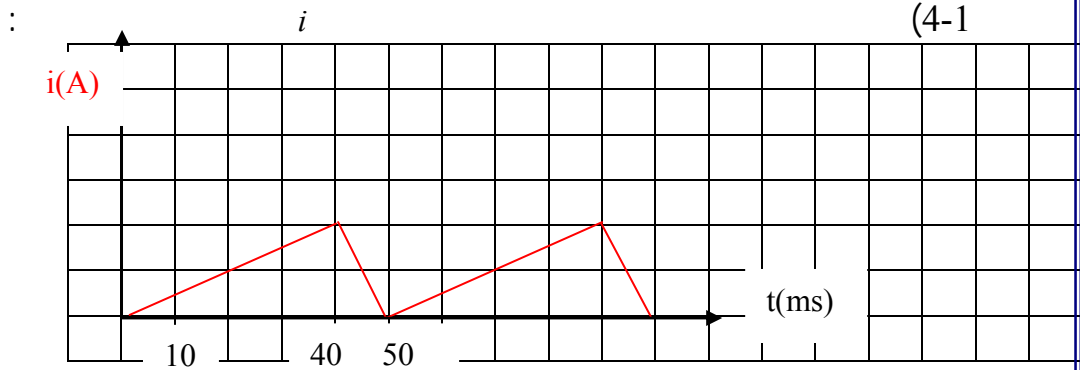

. [40,50ms] : [0,40ms] :

$u_{AC}$

$u_{AC}$

(


$u_{AC}$

(

. 0,25V / div

10ms / div :

:1-1 (1

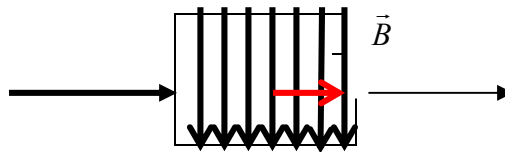

:2-1

: $\vec{B}$

. C A : \_\_\_\_\_ \*

: \_\_\_\_\_ \*

$$B = \mu_0 \cdot n \cdot I = 4 \cdot \pi \cdot 10^{-7} \cdot \frac{N}{\ell} \cdot I = 4 \cdot \pi \cdot 10^{-7} \cdot \frac{1000}{1} \cdot 5 = 6,28 \cdot 10^{-3} T$$

: $\vec{B}$


:3-1

$$\Phi = N.B.S = N.\mu_0.\frac{N}{\ell}S.I$$

$$L = N^2.\mu_0.\frac{S}{\ell} \quad ; \quad \Phi = L.I \quad ;$$

$$L = N^2.4.\pi.10^{-7}.\frac{\pi.r^2}{\ell} = 9,86 \times 10^{-3} H$$

: ( 2

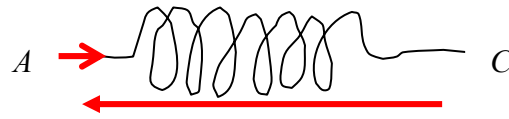

$$U_{AC} =$$

$i \quad U \quad ;$

$$e = -L \frac{di}{dt} \quad ; \quad \text{مع}$$

$$U_{AC} = ri + L \frac{di}{dt} \quad ; \quad \text{إن:}$$

$$U_{AC} = L \frac{di}{dt} \quad ;$$

$[0,40ms] \quad ; \quad \text{في المجال}^*$

$$i = at \quad ; \quad i = \frac{\Delta i}{\Delta t} = \frac{0,2 - 0}{(40 - 0) \times 10^{-3} s} = 50 A/s$$

$$\frac{di}{dt} = 50 \quad \leftarrow \quad \text{إن: } i = 50t$$

$$U_{AC} = L \frac{di}{dt} = 9,86 \times 10^{-3} \times 50 = 0,49V \quad ; \quad \text{وبالتالي}$$

$[40,50ms] \quad \text{وفي المجال}^*$

$$i = \alpha t + \beta \quad ; \quad \alpha = \frac{\Delta i}{\Delta t} = \frac{0,2A}{(50 - 40) \times 10^{-3} s} = -200$$

$$i = -200t + \beta \quad ; \quad \text{إن:}$$

$\beta$  تحديد

$$i = 0 \quad \text{لدينا } t = 50ms \quad ; \quad \text{عند اللحظة}$$

$$0 = -10 + \beta \quad ; \quad \text{إن: } 0 = -200 \times 50 \times 10^{-3} + \beta$$

ومنه:  $\beta = 10$

$$i = -200t + 10 \quad ; \quad \text{إن}$$


$$\frac{di}{dt} = -200$$

$$U_{AC} = L \frac{di}{dt} = 9,86 \times 10^{-3} \times (-200) = -1,97V$$

( 2

$0,5V \rightarrow 2div$

بالسلم

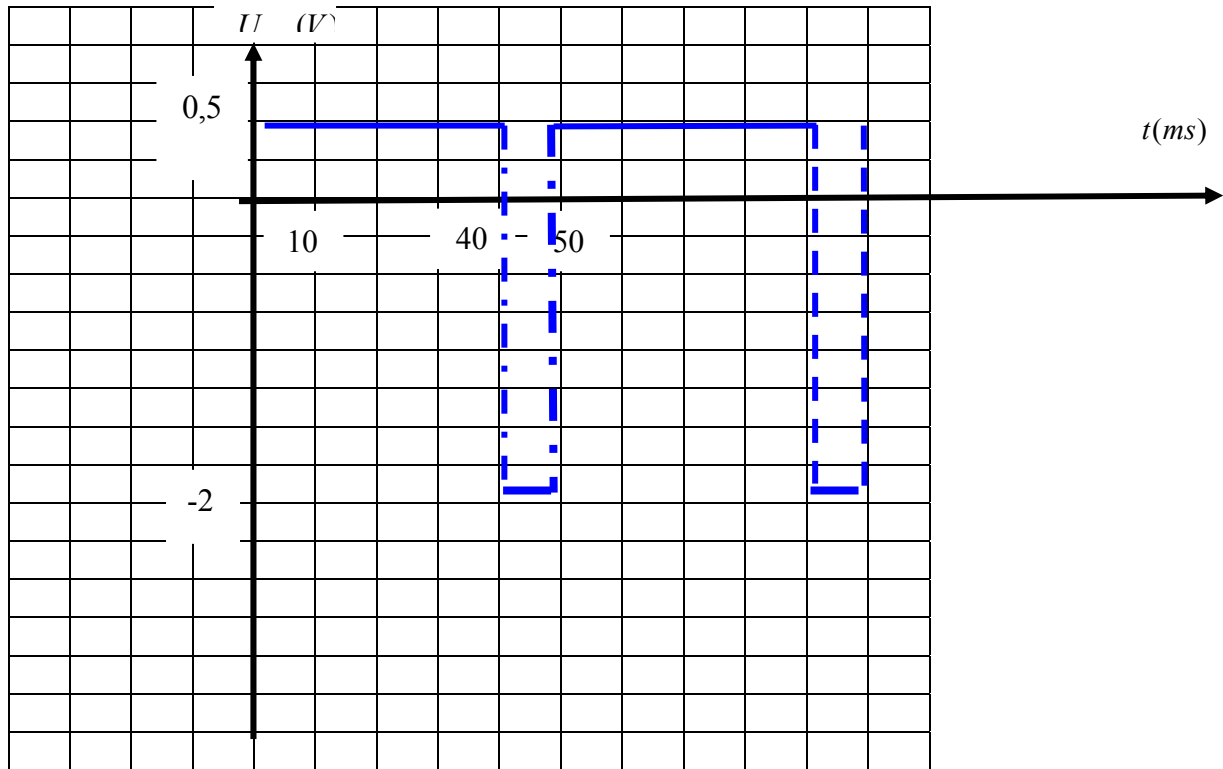


معا

Voir suite

(IV)

$R = 100\Omega$

G.B.F.

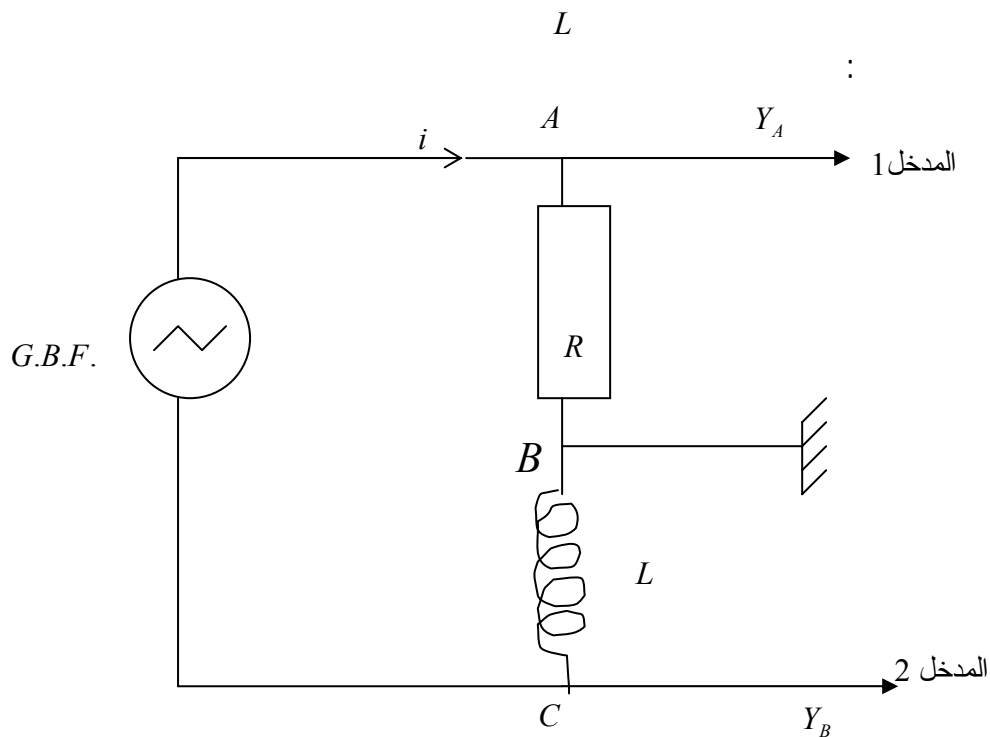

:  $Y_1$   
1  $u_{AB} = u_1$  :  
2  $u_{CB} = u_2$   
:  
 $1ms / div$  :  
 $1V / div$  : 1  
 $0,5v / div$  : 2  
:



$x'x$   
 $.i R u_1$  (1)


$$\frac{di}{dt} L u_2 \quad (2)$$

$$\frac{du_1}{dt}, L, R, u_2 \quad (3)$$

$$\quad \quad \quad (5)$$

$$\quad \quad \quad (6)$$

: \_\_\_\_\_  
(1)

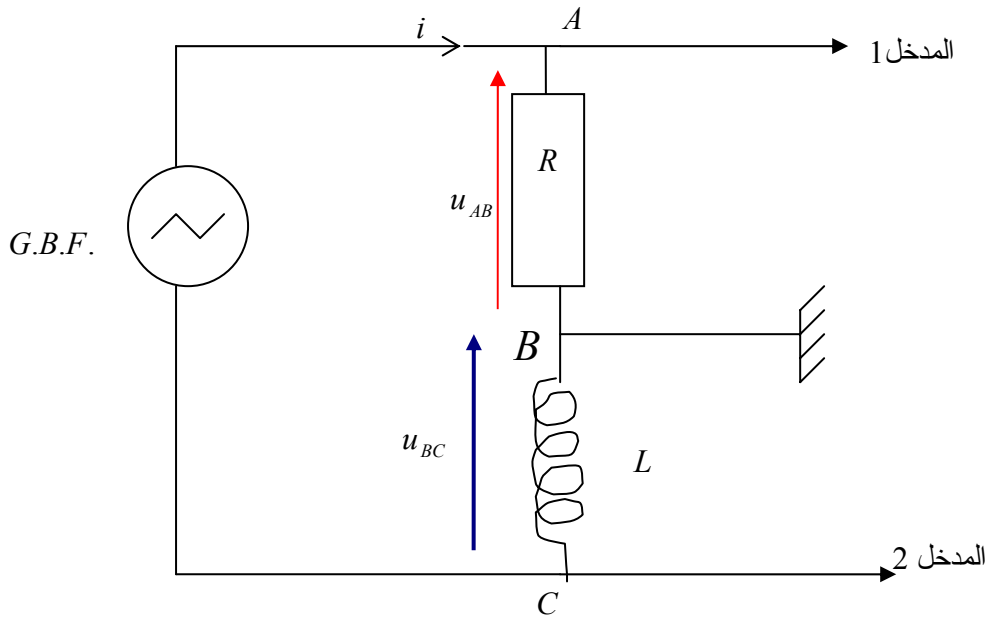

$$u_{AB} = Ri \quad (1)$$

$$u_{AB} = u_1 \quad :$$

$$u_1 = Ri$$

$$u_{BC} = ri - e$$

$$i \quad u \quad :$$

$$u_{BC} = -e$$

$$(e = -L \frac{di}{dt} \text{ مع})$$

$$u_{CB} = u_2 \quad :$$

$$u_2 = -u_{BC} = e = -L \frac{di}{dt} \quad :$$

$$u_2 = -L \frac{di}{dt}$$

$$u_1 = Ri \quad : \quad (3)$$

$$\frac{du_1}{dt} = R \frac{di}{dt}$$

$$: \quad \frac{di}{dt} = -\frac{u_2}{L} \quad :$$

$$\boxed{\frac{du_1}{dt} = -R \frac{u_2}{L}}$$

$$\boxed{L = \frac{-R.u_2}{\frac{du_1}{dt}}}$$

:

$$: \quad [0,1ms] \quad (4) \quad *$$

$$u_1 = \alpha t + \beta$$

$$\alpha = \frac{\Delta u_1}{\Delta t} = \frac{(0-4)A}{(1-0) \times 10^{-3} s} = -4 \times 10^3 A/s$$

$$u_1 = -4 \times 10^3 t + \beta$$

$$\frac{du_1}{dt} = -4 \times 10^3 :$$

$$u_2 = 2 \times 0,5V / div = 1V \quad :$$

:

$$L = -100 \times \frac{1}{4 \times 10^3} = 25 \times 10^{-3} H$$

$$Em = \frac{1}{2} L i^2 : \underline{\hspace{2cm}} \quad (5)$$

:

$$Em_{\max} = \frac{1}{2} L i_{\max}^2$$

$$i = \frac{u_1}{R} \quad :$$

$$i_{\max} = \frac{u_{1\max}}{R} = \frac{4}{100} = 0,04A \quad :$$

$$Em_{\max} = \frac{1}{2} L i_{\max}^2 = \frac{1}{2} \times 25 \times 10^{-3} \times (0,04)^2 = 2 \times 10^{-5} J$$

SBIRO Abdelkrim mail : sbiabdou@yahoo.fr

[www.madariss.fr](http://www.madariss.fr)